

Name: _____

Electricity

Choose the best answer for each question. Write the letter on the line.

- _____ 1. What supplies energy in an electric circuit?
- a. a conductor
 - b. light bulb
 - c. a wire
 - d. a battery



- _____ 2. Which material is a conductor?
- a. plastic
 - b. silver
 - c. glass
 - d. wood

- _____ 3. Which type of circuit is Circuit A?
- a. series
 - b. parallel
 - c. perpendicular
 - d. current

- _____ 4. Which item is a resistor in Circuit B?
- a. light bulb
 - b. wire
 - c. battery
 - d. screws

- _____ 5. Why did the person who made Circuit A probably connect the wires to a penny?
- a. They needed to use a penny to make the bulb light.
 - b. They were testing to see if the penny conducts electricity.
 - c. They used the penny to supply extra power.
 - d. The penny will prevent sparks.

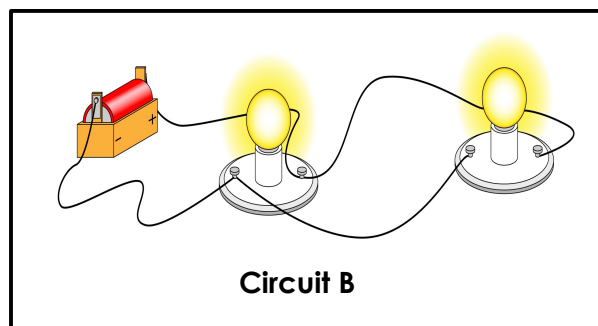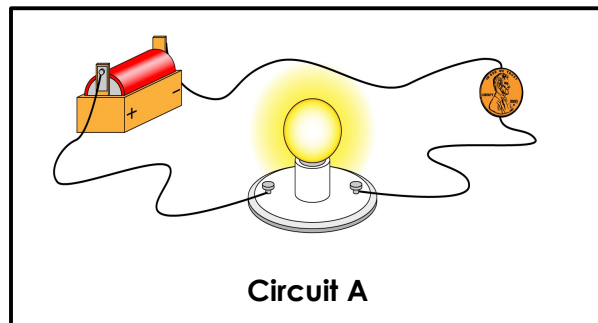- _____ 6. Which of these could be used as a resistor in a circuit?
- a. a pencil
 - b. a gas engine
 - c. a rubber eraser
 - d. an electric motor




ANSWER KEY

Electricity

Choose the best answer for each question. Write the letter on the line.


- d** 1. What supplies energy in an electric circuit?
- a. a conductor
 - b. light bulb
 - c. a wire
 - d. **a battery**

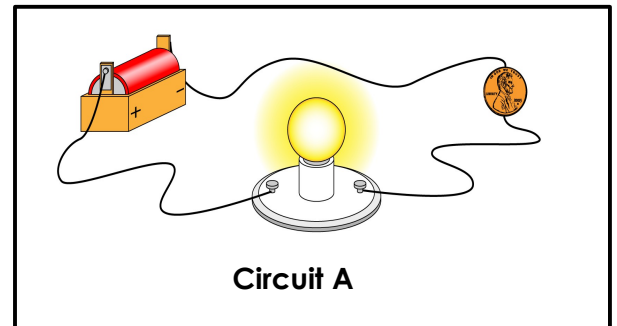- b** 2. Which material is a conductor?
- a. plastic
 - b. **silver**
 - c. glass
 - d. wood



- a** 3. Which type of circuit is Circuit A?
- a. **series**
 - b. parallel
 - c. perpendicular
 - d. current

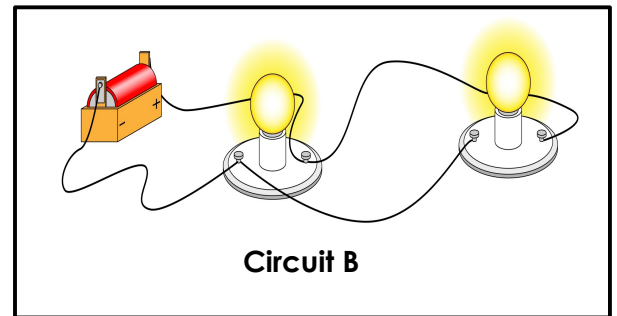- a** 4. Which item is a resistor in Circuit B?
- a. **light bulb**
 - b. wire
 - c. battery
 - d. screws



- b** 5. Why did the person who made Circuit A probably connect the wires to a penny?
- a. They needed to use a penny to make the bulb light.
 - b. **They were testing to see if the penny conducts electricity.**
 - c. They used the penny to supply extra power.
 - d. The penny will prevent sparks.

- d** 6. Which of these could be used as a resistor in a circuit?
- a. a pencil
 - b. a gas engine
 - c. a rubber eraser
 - d. **an electric motor**